

Project (1)
Spartan6 - DSP48A1

Abdullah Mohammed Ahmed Mahmoud
Under the Supervision
Eng. Kareem Wassem

August 2024

RTL Code For the Design and Mux

Mux Code

```
1 module reg_mux(rst, clk, ce, sel, in, out_mux);
2     parameter reg_size = 18;
3     parameter RST_TYPE = "SYNC";
4     input rst, clk, ce, sel;
5     input [reg_size-1:0] in;
6     output wire [reg_size-1:0] out_mux;
7     reg [reg_size-1:0] out_ff;
8
9     generate
10         if (RST_TYPE == "SYNC") begin
11             always @(posedge clk) begin
12                 if (rst)
13                     out_ff <= {reg_size{1'b0}};
14                 else if (ce)
15                     out_ff <= in;
16             end
17         end else begin
18             always @(posedge clk or posedge rst) begin
19                 if (rst)
20                     out_ff <= {reg_size{1'b0}};
21                 else if (ce)
22                     out_ff <= in;
23             end
24         end
25     endgenerate
26
27     assign out_mux = (sel) ? out_ff : in;
28 endmodule
```

Design Code

```
1 module firstDSP(A, B, C, D, CARRYIN, clk, opmode, BCIN,
2     CEA, CEB, CEC, CECARRYIN, CED, CEM, CEOPMODE, CEP,
3     RSTA, RSTB, RSTC, RSTCARRYIN, RSTD, RSTM, RSTOPMODE, RSTP,
4     BCOUT, PCIN, PCOUT, M, P, CARRYOUT, CARRYOUTF);
5
6     parameter AOREG = 0;
7     parameter A1REG = 1;
8     parameter BOREG = 0;
9     parameter B1REG = 1;
10    parameter CREG = 1;
11    parameter DREG = 1;
12    parameter MREG = 1;
13    parameter PREG = 1;
14    parameter CARRYINREG = 1;
15    parameter CARRYOUTREG = 1;
16    parameter OPMODEREG = 1;
17    parameter CARRYINSEL = "OPMODE5";
18    parameter B_INPUT = "DIRECT";
19    parameter RSTTYPE = "SYNC";
20
21    input clk, CEA, CEB, CEC, CECARRYIN, CED, CEM, CEOPMODE, CEP;
22    input RSTA, RSTB, RSTC, RSTCARRYIN, RSTD, RSTM, RSTOPMODE, RSTP, CARRYIN;
23    input [7:0] opmode;
24    input [17:0] A, B, D, BCIN;
25    input [47:0] C, PCIN;
26    output CARRYOUT, CARRYOUTF;
27    output [17:0] BCOUT;
28    output [35:0] M;
29    output [47:0] P, PCOUT;
30
31    wire CYI, CIN, carryout_postsum;
```

```

32 wire [7:0] opmode_mux;
33 wire [17:0] A0, A1, B0, B1, D_mux, B_mux, PRE_SUM, B0_mux;
34 wire [35:0] prod;
35 wire [47:0] C_mux, conc_signal, post_sum;
36 reg [47:0] X_mux, Z_mux;
37
38 assign CYI = (CARRYINSEL == "OPMODE5") ? opmode_mux[5] : (CARRYINSEL == "CARRYIN") ?
  CARRYIN : 0;
39 assign B_mux = (B_INPUT == "DIRECT") ? B : (B_INPUT == "CASCADE") ? BCIN : 0;
40 assign PRE_SUM = (opmode_mux[6]) ? D_mux - B0 : D_mux + B0;
41 assign B0_mux = (opmode_mux[4]) ? PRE_SUM : B0;
42 assign conc_signal = {D_mux[11:0], A1, B1};
43 assign prod = A1 * B1;
44 assign BCOUT = B1;
45 assign {carryout_postsum, post_sum} = (opmode_mux[7]) ? (Z_mux - (X_mux + CIN)) : (
  Z_mux + X_mux + CIN);
46 assign CARRYOUTF = CARRYOUT;
47 assign PCOUT = P;
48
49 reg_mux #(.reg_size(18), .RST_TYPE(RSTTYPE)) A0_REG (RSTA, clk, CEA, AOREG, A, A0);
50 reg_mux #(.reg_size(18), .RST_TYPE(RSTTYPE)) A1_REG (RSTA, clk, CEA, A1REG, A0, A1);
51 reg_mux #(.reg_size(18), .RST_TYPE(RSTTYPE)) B0_REG (RSTB, clk, CEB, AOREG, B_mux,
  B0);
52 reg_mux #(.reg_size(18), .RST_TYPE(RSTTYPE)) B1_REG (RSTB, clk, CEB, A1REG, B0_mux,
  B1);
53 reg_mux #(.reg_size(18), .RST_TYPE(RSTTYPE)) D_REG (RSTD, clk, CED, DREG, D, D_mux);
54 reg_mux #(.reg_size(48), .RST_TYPE(RSTTYPE)) C_REG (RSTC, clk, CEC, CREG, C, C_mux);
55 reg_mux #(.reg_size(8), .RST_TYPE(RSTTYPE)) OPMODE_REG (RSTOPMODE, clk, CEOPMODE,
  OPMODEREG, opmode, opmode_mux);
56 reg_mux #(.reg_size(36), .RST_TYPE(RSTTYPE)) M_REG (RSTM, clk, CEM, MREG, prod, M);
57 reg_mux #(.reg_size(1), .RST_TYPE(RSTTYPE)) CARRYIN_REG (RSTCARRYIN, clk, CECARRYIN,
  CARRYINREG, CYI, CIN);
58 reg_mux #(.reg_size(1), .RST_TYPE(RSTTYPE)) CARRYOUT_REG (RSTCARRYOUT, clk,
  CECARRYOUT, CARRYOUTREG, carryout_postsum, CARRYOUT);
59 reg_mux #(.reg_size(48), .RST_TYPE(RSTTYPE)) P_REG (RSTP, clk, CEP, PREG, post_sum,
  P);
60
61 always @(*) begin
62     case ({opmode_mux[1], opmode_mux[0]})
63         2'b00: X_mux = 0;
64         2'b01: X_mux = M;
65         2'b10: X_mux = PCOUT;
66         2'b11: X_mux = conc_signal;
67     endcase
68 end
69
70 always @(*) begin
71     case ({opmode_mux[3], opmode_mux[2]})
72         2'b00: Z_mux = 0;
73         2'b01: Z_mux = PCIN;
74         2'b10: Z_mux = P;
75         2'b11: Z_mux = C_mux;
76     endcase
77 end
78 endmodule

```

TestBench

```

1 module firstDSP_tb();
2     reg clk, CEA, CEB, CEC, CECARRYIN, CED, CEM, CEOPMODE, CEP;
3     reg RSTA, RSTB, RSTC, RSTCARRYIN, RSTD, RSTM, RSTOPMODE, RSTP, CARRYIN;
4     reg [7:0] opmode;
5     reg [17:0] A, B, D, BCIN;

```

```

6  reg [47:0] C, PCIN;
7  wire CARRYOUT, CARRYOUTF, CARRYOUT_2, CARRYOUTF_2;
8  wire [17:0] BCOUT, BCOUT_2;
9  wire [35:0] M, M2;
10 wire [47:0] P, P_2, PCOUT, PCOUT_2;
11
12 // Instantiate the first DUT with default parameters
13 firstDSP dut (
14     .A(A), .B(B), .C(C), .D(D), .CARRYIN(CARRYIN), .clk(clk), .opmode(opmode), .BCIN
15     (BCIN),
16     .CEA(CEA), .CEB(CEB), .CEC(CEC), .CECARRYIN(CECARRYIN), .CED(CED), .CEM(CEM), .
17     CEOPMODE(CEOPMODE), .CEP(CEP),
18     .RSTA(RSTA), .RSTB(RSTB), .RSTC(RSTC), .RSTCARRYIN(RSTCARRYIN), .RSTD(RSTD), .
19     RSTM(RSTM), .RSTOPMODE(RSTOPMODE), .RSTP(RSTP),
20     .BCOUT(BCOUT), .PCIN(PCIN), .PCOUT(PCOUT), .M(M), .P(P), .CARRYOUT(CARRYOUT), .
21     CARRYOUTF(CARRYOUTF)
22 );
23
24 // Instantiate the second DUT with modified parameters
25 firstDSP #(
26     .CARRYINSEL("CARRYIN"), .B_INPUT("CASCADE"), .RSTTYPE("ASYNC")
27 ) dut_2 (
28     .A(A), .B(B), .C(C), .D(D), .CARRYIN(CARRYIN), .clk(clk), .opmode(opmode), .BCIN
29     (BCIN),
30     .CEA(CEA), .CEB(CEB), .CEC(CEC), .CECARRYIN(CECARRYIN), .CED(CED), .CEM(CEM), .
31     CEOPMODE(CEOPMODE), .CEP(CEP),
32     .RSTA(RSTA), .RSTB(RSTB), .RSTC(RSTC), .RSTCARRYIN(RSTCARRYIN), .RSTD(RSTD), .
33     RSTM(RSTM), .RSTOPMODE(RSTOPMODE), .RSTP(RSTP),
34     .BCOUT(BCOUT_2), .PCIN(PCIN), .PCOUT(PCOUT_2), .M(M2), .P(P_2), .CARRYOUT(
35     CARRYOUT_2), .CARRYOUTF(CARRYOUTF_2)
36 );
37
38 // Clock generation
39 initial begin
40     clk = 1;
41     forever #2 clk = ~clk;
42 end
43
44 integer i;
45
46 // Initial block for reset and testing
47 initial begin
48     // Apply reset
49     RSTA = 1; RSTB = 1; RSTC = 1; RSTCARRYIN = 1;
50     RSTD = 1; RSTM = 1; RSTOPMODE = 1; RSTP = 1;
51     for (i = 0; i < 10; i = i + 1) begin
52         @(negedge clk);
53         A = $random; B = $random; C = $random; D = $random; BCIN = $random; PCIN =
54         $random; opmode = $random;
55         CARRYIN = $random; CEA = $random; CEB = $random; CEC = $random; CECARRYIN =
56         $random;
57         CED = $random; CEM = $random; CEP = $random; CEOPMODE = $random;
58         #5;
59         // Testing internal synchronous reset
60         if (dut.B1 != 0 || dut.A1 != 0 || dut.D_mux != 0 || dut.C_mux != 0 ||
61             dut.opmode_mux != 0 || dut.M != 0 || dut.CIN != 0 || dut.CARRYOUT != 0
62             || dut.P != 0) begin
63             $display("Error in SYNCH RESET functionality");
64             $stop;
65         end
66         // Testing internal asynchronous reset
67         if (dut_2.B1 != 0 || dut_2.A1 != 0 || dut_2.D_mux != 0 || dut_2.C_mux != 0
68             ||
69             dut_2.opmode_mux != 0 || dut_2.M != 0 || dut_2.CIN != 0 || dut_2.
70             CARRYOUT != 0 || dut_2.P != 0) begin

```

```

58         $display("Error in ASYNCH RESET functionality");
59         $stop;
60     end
61 end
62 $display("RESET TEST PASSED");
63
64 // Deassert reset
65 RSTA = 0; RSTB = 0; RSTC = 0; RSTCARRYIN = 0;
66 RSTD = 0; RSTM = 0; RSTOPMODE = 0; RSTP = 0;
67 CEA = 0; CEB = 0; CEC = 0; CECARRYIN = 0; CED = 0; CEM = 0; CEOPMODE = 0; CEP =
0;
68 for (i = 0; i < 10; i = i + 1) begin
69     @(negedge clk);
70     A = $random; B = $random; C = $random; D = $random; BCIN = $random; PCIN =
$random; opmode = $random;
71     CARRYIN = $random;
72     #5;
73     // Testing clock enable with synchronous reset
74     if (dut.B1 != 0 || dut.A1 != 0 || dut.D_mux != 0 || dut.C_mux != 0 ||
75         dut.opmode_mux != 0 || dut.M != 0 || dut.CIN != 0 || dut.CARRYOUT != 0
|| dut.P != 0) begin
76         $display("Error in CLOCK ENABLE functionality");
77         $stop;
78     end
79     // Testing clock enable with asynchronous reset
80     if (dut_2.B1 != 0 || dut_2.A1 != 0 || dut_2.D_mux != 0 || dut_2.C_mux != 0
||
81         dut_2.opmode_mux != 0 || dut_2.M != 0 || dut_2.CIN != 0 || dut_2.
CARRYOUT != 0 || dut_2.P != 0) begin
82         $display("Error in CLOCK ENABLE functionality");
83         $stop;
84     end
85 end
86 $display("CLOCK ENABLE TEST PASSED");
87
88 // Testing specific functional cases
89 @(negedge clk);
90 CEA = 1; CEB = 1; CEC = 1; CECARRYIN = 1; CED = 1; CEM = 1; CEOPMODE = 1; CEP =
1;
91 A = 1; B = 2; C = 3; D = 4; opmode = 8'b00111101; BCIN = 5; CARRYIN = 0;
92 repeat (5) @(negedge clk);
93
94 opmode = 8'b00000011; BCIN = 10; CARRYIN = 1;
95 repeat (5) @(negedge clk);
96
97 opmode = 8'b10011010; BCIN = 5; CARRYIN = 0;
98 repeat (5) @(negedge clk);
99
100 opmode = 8'b10100101; BCIN = 10; CARRYIN = 0; PCIN = 100;
101 repeat (10) @(negedge clk);
102
103 $stop;
104 end
105 endmodule

```

Simulation on Questa Sim

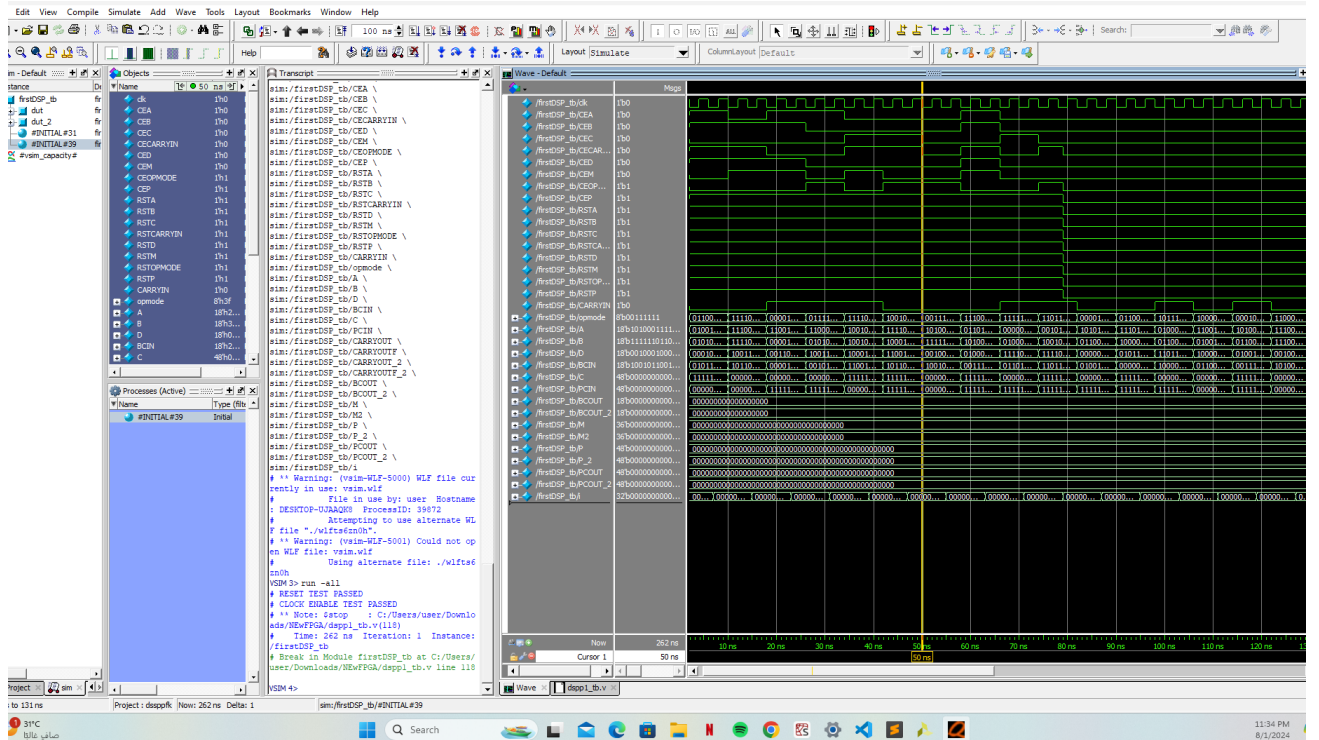


Figure 1: A snippet of the design's testbench simulation.

Do File

```

1 vsim -voptargs=+acc work.firstDSP_tb
2 add wave -position insertpoint \
3 sim:/firstDSP_tb/clk \
4 sim:/firstDSP_tb/CEA \
5 sim:/firstDSP_tb/CEB \
6 sim:/firstDSP_tb/CEC \
7 sim:/firstDSP_tb/CECARRYIN \
8 sim:/firstDSP_tb/CED \
9 sim:/firstDSP_tb/CEM \
10 sim:/firstDSP_tb/CEOPMODE \
11 sim:/firstDSP_tb/CEP \
12 sim:/firstDSP_tb/RSTA \
13 sim:/firstDSP_tb/RSTB \
14 sim:/firstDSP_tb/RSTC \
15 sim:/firstDSP_tb/RSTCARRYIN \
16 sim:/firstDSP_tb/RSTD \
17 sim:/firstDSP_tb/RSTM \
18 sim:/firstDSP_tb/RSTOPMODE \
19 sim:/firstDSP_tb/RSTP \
20 sim:/firstDSP_tb/CARRYIN \
21 sim:/firstDSP_tb/opmode \
22 sim:/firstDSP_tb/A \
23 sim:/firstDSP_tb/B \
24 sim:/firstDSP_tb/D \
25 sim:/firstDSP_tb/BCIN \
26 sim:/firstDSP_tb/C \
27 sim:/firstDSP_tb/PCIN \
28 sim:/firstDSP_tb/CARRYOUT \
29 sim:/firstDSP_tb/CARRYOUTF \

```

```

30 sim:/firstDSP_tb/CARRYOUT_2 \
31 sim:/firstDSP_tb/CARRYOUTF_2 \
32 sim:/firstDSP_tb/BCOUT \
33 sim:/firstDSP_tb/BCOUT_2 \
34 sim:/firstDSP_tb/M \
35 sim:/firstDSP_tb/M2 \
36 sim:/firstDSP_tb/P \
37 sim:/firstDSP_tb/P_2 \
38 sim:/firstDSP_tb/PCOUT \
39 sim:/firstDSP_tb/PCOUT_2 \
40 sim:/firstDSP_tb/i
41 run -all

```

Vivado Simulation and Synthesis for the DSP

I have added a constraint file with the following:

```

1 # Define a clock with a period of 10 ns (100 MHz) on pin W5
2 create_clock -period 10.0 [get_ports clk]
3
4 # Set the pin location and I/O standard for the clock
5 set_property PACKAGE_PIN W5 [get_ports clk]
6 set_property IOSTANDARD LVCMOS33 [get_ports clk]

```

Then, I clicked on the run synthesis and also did a report timing summary for the design, here are the results:

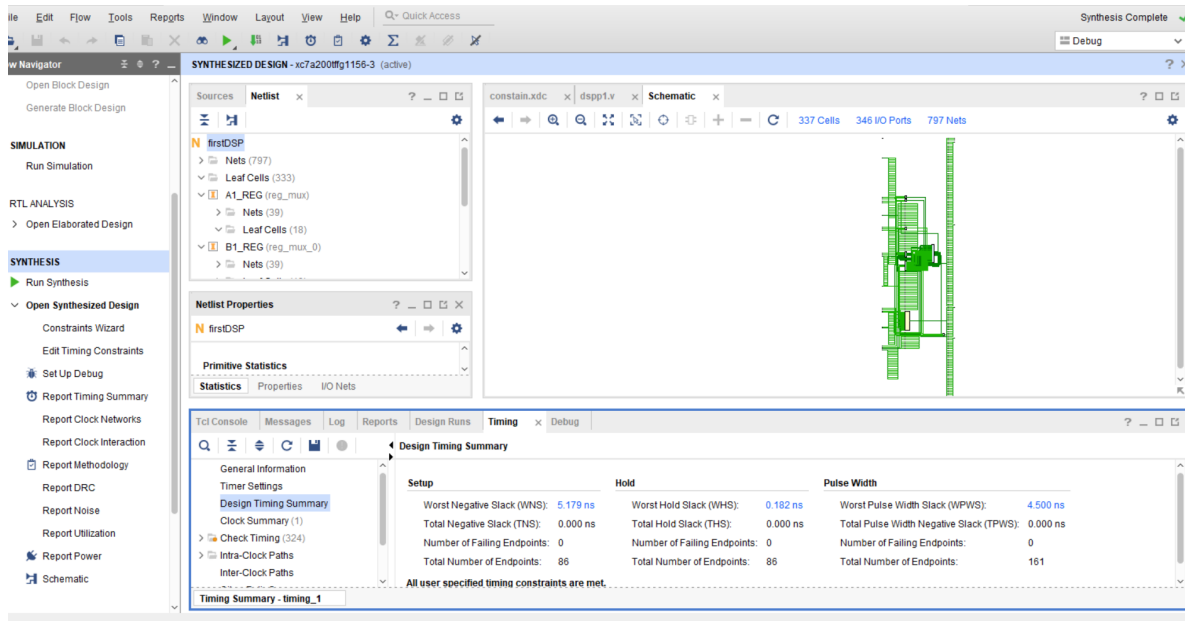


Figure 2: The Schematic of the design with the report timing summary.


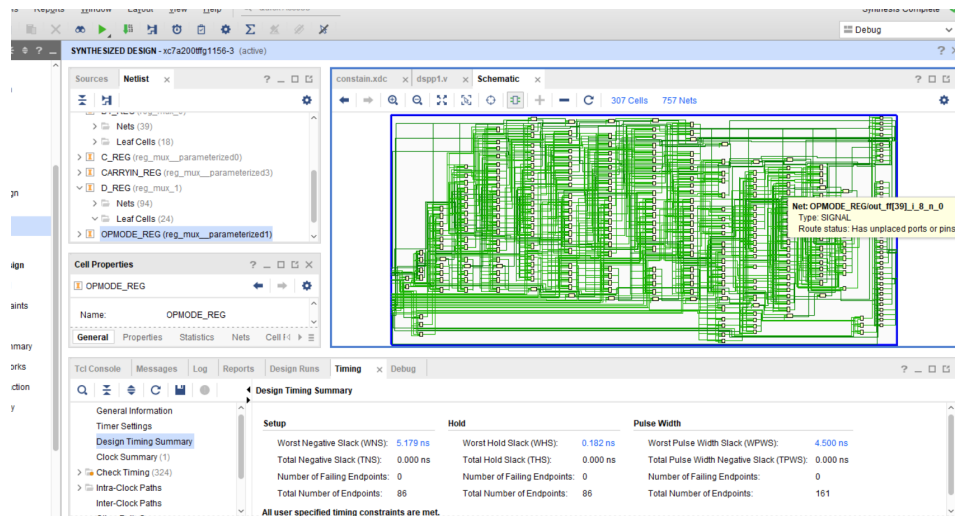



Figure 3: Inside the design of the opmode.

 

Figure 4: The messages bar shows no critical errors.



(a) Timing

 

(b) Utilization Report

Figure 5: The Utilization and Timing Before Implementation.

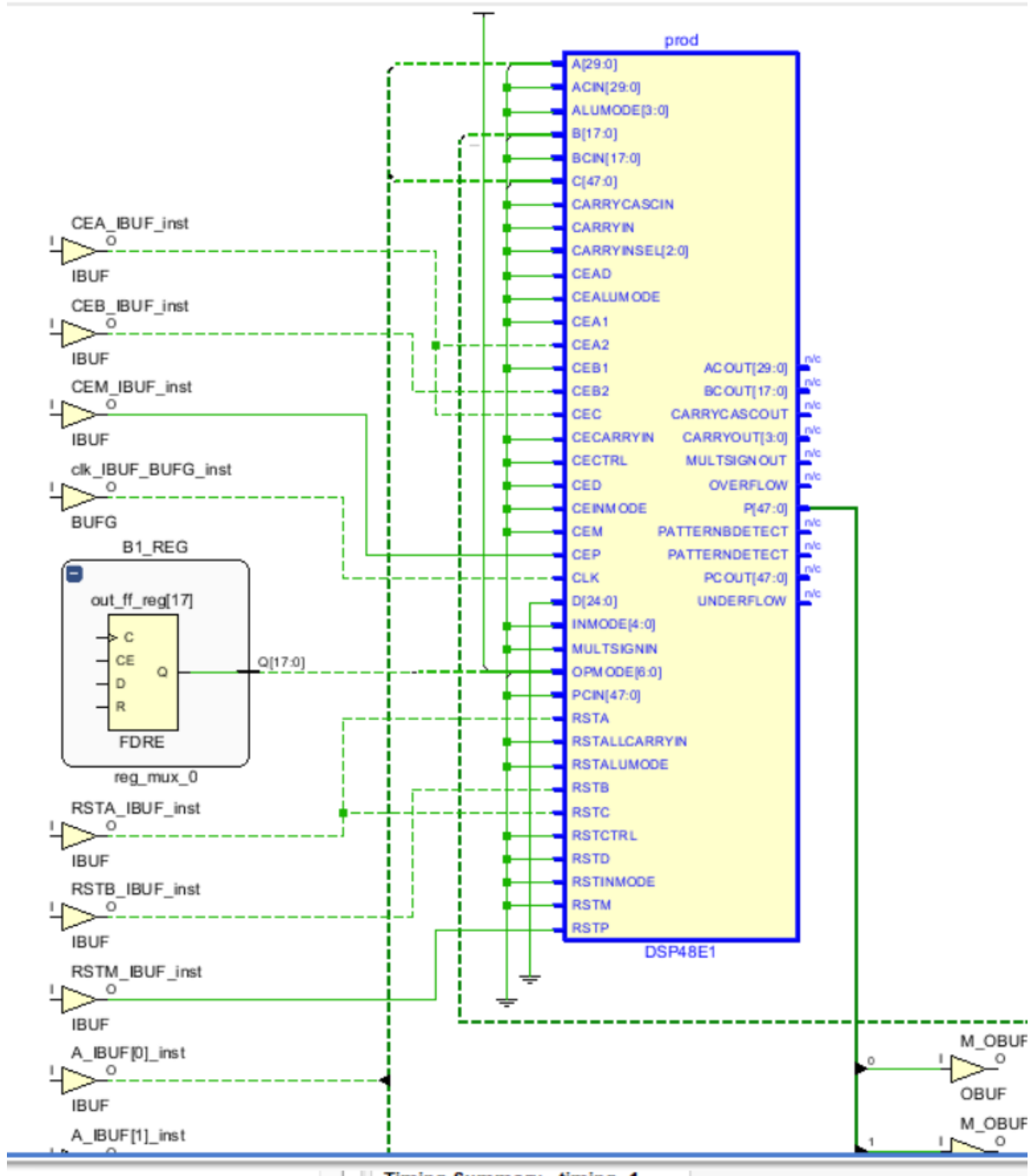


Figure 6: The DSP48A1

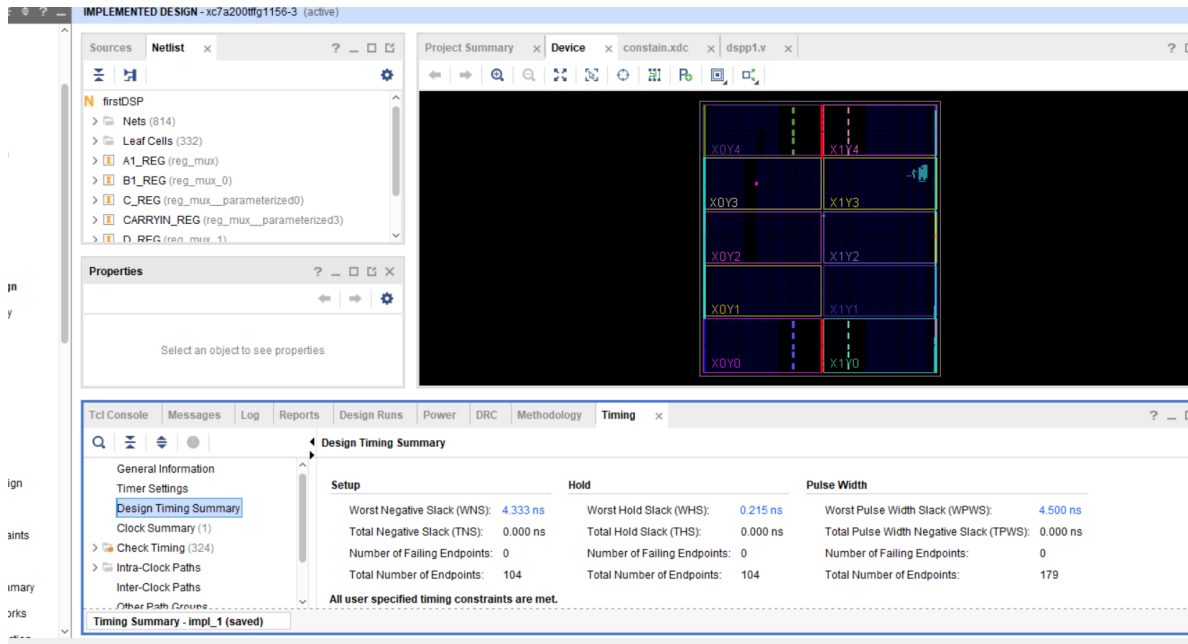


Figure 7: The Implementation Design after running it.

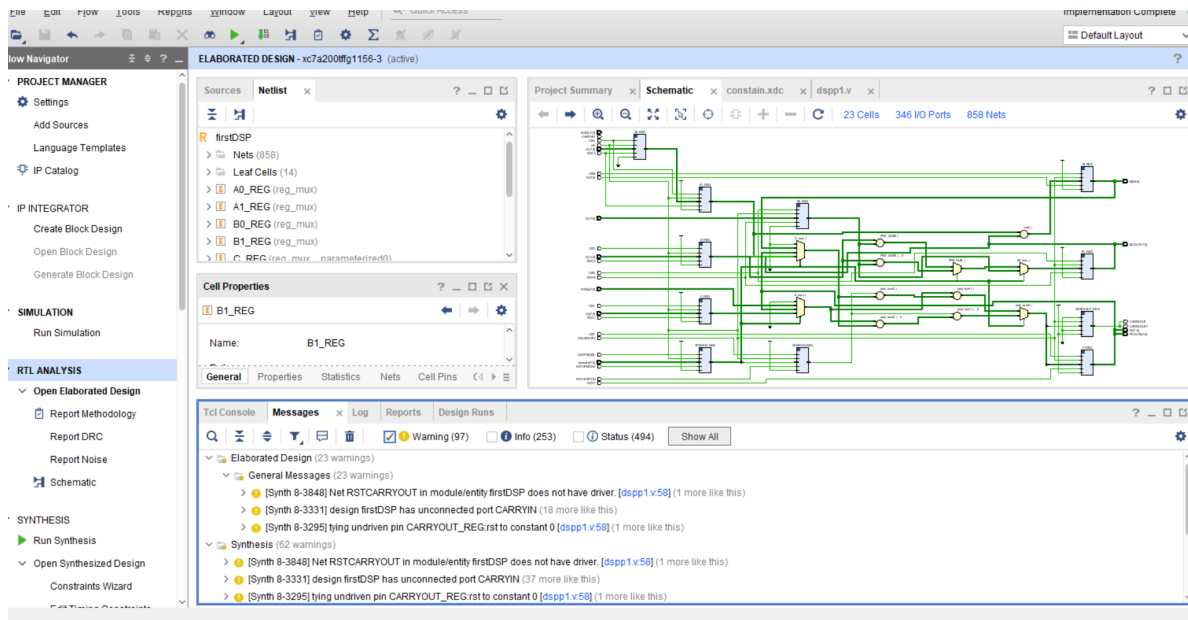


Figure 8: The Elaborated Design